

Working Principle of Optocoupler Circuit Module



Overview

Optocoupler Tutorial and Optocoupler Application Optocoupling devices work as logic level changeovers between two circuits, It has the ability to block noise.

Key Takeaways

An optocoupler circuit module transfers electrical signals between isolated circuits using light, providing electrical isolation while allowing signal control across different voltage domains.

Overview and Function

An optocoupler, also called a photocoupler or opto-isolator, is a device that transfers an electrical signal from one circuit to another without a direct electrical connection. It achieves this by converting the input electrical signal into light using an infrared LED, which then activates a phototransistor on the output side, converting the light back into an electrical signal. This optical coupling ensures galvanic isolation, protecting sensitive components and preventing noise or voltage spikes from propagating between circuits.

Construction

A typical optocoupler module, such as the PC817 or HY-M154, contains: An IR LED on the input side. A phototransistor on the output side. Supporting circuitry like resistors and jumpers for configuring input/output connections.

Multiple channels (e.g., 2, 4, or 8) for handling several isolated signals simultaneously.

The LE

D emits infrared light proportional to the input current. The phototransistor absorbs this light, generating a corresponding output current. The Current Transfer Ratio (CTR), defined as the ratio of output current to input current, is a key parameter affecting module performance.

Applications

Optocoupler modules are widely used for:

- Voltage level shifting: Converting signals from one voltage domain to another, e.g., 12V to 5V for microcontrollers.
- Signal isolation: Protecting microcontrollers or sensitive electronics from high-voltage circuits.
- Noise reduction: Preventing electrical noise from propagating between circuits.

Digital input/output interfacing: Modules can act as digital input boards, detecting whether a circuit is active and sending a corresponding signal to a microcontroller.

Wiring and Usage

When using a module like the PC817: The input-side VCC/GND and output-side VCC/GND are completely separate; do not connect them together. Input signals typically activate the LED when pulled LOW, causing the phototransistor to conduct and produce an output signal. Modules often include jumpers to connect or isolate input and output grounds, allowing flexible configuration for fully isolated or partially connected systems.

Proper resistor selection is important to set the correct LED current and output voltage levels, ensuring reliable operation and matching the CTR to the application.

Summary

Optocoupler modules provide a simple and effective way to interface circuits with different voltages, protect sensitive electronics, and reduce noise. By understanding the LED-phototransistor operation, CTR, and proper wiring, these modules can be integrated into a wide range of applications, from microcontroller signal interfacing to industrial control systems.

Article Content

Optocoupler Tutorial and Optocoupler Application

Optocoupling devices work as logic level changeovers between two circuits, It has the ability to block noise transfer across the integrated circuits, for isolating logic levels from high voltage

Optocoupler Tutorial for Beginners

An optocoupler (or opto-isolator) is a component that transfer signals between circuits using light. In this guide, you'll learn how they work and how you can use one in your own projects.

ANO007 | Understanding Phototransistor Optocouplers

In order to design a functionally robust and reliable application with optocouplers, it is essential to understand not only the device's main parameters and parasitic elements, but also their tolerances

Using Opto Couplers

The main purpose of an optocoupler interface is to completely isolate the input circuit from the output circuit, which normally means there will be two completely separate power supplies, one for the input

Optocoupler Working Principle: Types, CTR Formula and Industrial ...

An optocoupler (also called a photocoupler, opto-isolator or optical coupler) is a semiconductor device that transfers electrical signals between two electrically isolated circuits using

Optocouplers Guide: Understanding Types, Applications, and Circuit ...

Learn how optocouplers ensure electrical isolation and signal transfer in circuits. This guide covers their components, working principles, and applications. An optocoupler, also known as

Optocouplers 101: A Comprehensive Guide for PCB

In this comprehensive blog, we'll dive deep into optocoupler basics, their working principle, types, applications in PCB design, and advantages,

What is Optocoupler and How it works?

These components are called optocouplers or optoisolators or simply optos, and they perform the crucial function of passing signals between isolated sections of circuitry. They use light to

Corechips Electronic

Aluminum foil is the main material of aluminum electrolytic capacitors. In order to increase the contact area between aluminum foil and electrolyte, the surface The working principle of optoisolators!

IR Sensors: Working Principles, Module, and Types

Learn about IR sensors, their working principle, types, pinouts, applications, and more. Explore how infrared sensors work and their uses in various modules.

How Optocouplers Work

FREE COURSE!! Learn about optocouplers. We'll look at how they are used to control circuits, how they work and also how to design some simple optocoupler circuits to show the working

How Optocouplers work

Optocoupler. In this video we learn how optocouplers work and also look at some simple electron circuits you can make yourself to understand how an optocoupler, opto-isolator, phototransistor ...

Optoelectronics: Optocouplers

Assembling these two components into an integrated circuit (IC) package gives us a basic optocoupler. Before investigating commercially manufactured optocouplers, let's explore what is

Opto Coupled Devices

In this case the optocoupler will be used in Saturation Mode. A switched mode power supply may need a DC sample voltage of varying value to be fed back from the output to a voltage control system in the

What are Optocouplers? Definition, construction and working of ...

Working Of an Optocoupler An Optocoupler is a combination of LED and a Photo-diode packed in a single package. As we can see in the below-shown circuit diagram, when a high voltage appears

What Is Optocoupler and Its Application with Examples

Video: How an Optocoupler Works and Example Circuit II Photocouplers, Opto-couplers & Opto-isolators These devices are known by a

Optocoupler Types, Applications with Examples and Circuit Diagrams

Different Types of Optocoupler 1. Photo-Transistor Optocoupler A photo-transistor optocoupler works by using light to pass a signal between two separate parts of a circuit without any

ANO007 | Understanding Phototransistor Optocouplers

01. INTRODUCTION An optocoupler, also known as photocoupler or opto-isolator, is a device which can transfer an electrical signal across two galvanically-isolated circuits by way of optical coupling. Unlike

Related Video Reference

This video was associated with the source search result. Verify technical details against current product documentation and project requirements.

Contact Us

Continue your research online:

Website: <https://bagyou.es>

Technical inquiry: <https://bagyou.es/project-enquiry.html>

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.

