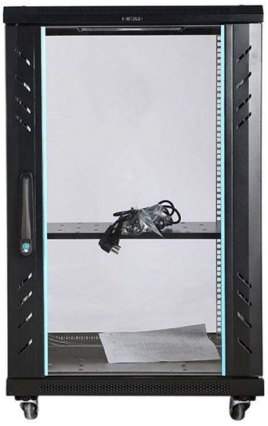
Design of wiring diagram for a three-level distribution box



Overview

Learn about the wiring process for a 3 phase distribution board (DB) box, including the necessary steps and safety precautions.

Key Takeaways

A three-level (three-phase) distribution box connects the main supply to MCBs and RCCBs, distributing power safely to multiple loads with proper neutral and earth connections.

Main Components and Connections

Incoming Supply: Connect the three-phase input (L1, L2, L3) from the transformer or main supply to the MCCB (Main Circuit Breaker) input. The neutral wire should be connected to the neutral busbar, and the earth wire to the earth busbar.

MC

Bs and RCCBs: The output of the MCCB feeds the MCBs (Miniature Circuit Breakers) for individual loads.

If RCC

Bs (Residual Current Circuit Breakers) are used, they are installed after the MCCB. For split-load boards, one RCCB can protect the left-side MCBs and another the right-side MCBs. Ensure the total RCCB rating is equal to or higher than the MCCB rating.

© 2026 BAGYOU FIBRE NETWORKS · All rights reserved

Load Connections: Connect each load's three-phase wires to the output of the corresponding three-pole MCB. If the load requires neutral, connect it to the neutral busbar. Connect the load's earth wire to the earth busbar.

Busbar Layout: Typically, MCBs are arranged in two rows (left and right). Each row can be connected to a separate RCCB if required. Phase colors often follow IEC standards: L1 – Brown, L2 – Black, L3 – Gray, Neutral – Blue, Earth – Green/Yellow.

Optional Split-

Load Configuration: For split-load boards, some MCBs can be connected to one RCCB and others to a second RCCB to separate critical and non-critical loads. This ensures selective protection and easier maintenance.

Safety Considerations

Always verify the current ratings of MCCB, MCBs, and RCCBs to match the load requirements. Ensure proper earthing to prevent electric shock. Neutral may be optional for purely three-phase loads but is required for mixed single-phase loads.

Electrical work should only be performed by a qualified electrician to avoid hazards. This wiring setup ensures safe and organized distribution of three-phase power to multiple loads, with protection against overloads, short circuits, and earth faults.

Article Content

Three (3) Phase Distribution Board Wiring Diagram and Connection

The three-phase distribution board is carefully designed to receive electrical power from a three-phase supply and distribute it to multiple circuits across all three phases to maintain balance

Step-by-Step Guide to Wiring a 3 Phase DB Box

Learn about the wiring process for a 3 phase distribution board (DB) box, including the necessary steps and safety precautions. Understand how to connect the incoming power supply, distribute it to

How to Wire 3-Phase, 400V Distribution Board? IEC

Below is three phase distribution board wiring diagram shown. The wiring connection is started from the main 600 A MCCB circuit breaker. The main 3 phase four wire supply enters the

Three Phase Distribution Board Wiring Guide

© 2026 BAGYOU FIBRE NETWORKS - All rights reserved

This document provides instructions for wiring a three phase distribution board for electrical power and lighting installation. It lists the required accessories including a 12-way three row distribution board

DIY Wiring a Three Phase Consumer Unit-Distribution Board and

Wiring a Three Phase Distribution Board is of a necessity when the Power Distribution requirement cannot be handled by a Single Phase Power Supply.

Wiring Diagram Of A 3 Phase Distribution Board

Understanding the wiring diagram of a three-phase distribution board is essential for anyone dealing with the installation and maintenance of an electrical system.

Three Phase Electrical Wiring Installation in Home

In our today electrical wiring installation tutorial, we will show how to wire and install a Three Phase distribution board and Consumer Unit from utility pole to a 3-Phase Energy Meter & 3-Phase

3 Phase Panel Board Wiring Diagram with Protection and Load Guide

Learn 3-phase panel board wiring with circuit breakers, protective relays, busbar, and load connections for safe and efficient electrical distribution.

Printed circuit board

In radio-frequency and fast switching circuits the inductance and capacitance of the printed circuit board conductors become significant circuit elements, usually

Paul Herber

370 Visio shapes and symbols in 19 Visio stencils (in both US units and metric units, in Visio VSSX format) for you to create drawings of domestic and industrial electrical installations, lighting plans,

WORLD WIDE WEB JOURNAL Home

By clicking download, will open to start the export process. The process may take but once it finishes a file will be downloadable from your browser. You may continue to browse the DL while the export

How to Wire 3-Phase, 400V Distribution Board? IEC

How to Wire 120V & 240V Main Panel? Breaker Box Installation How to Wire 208V & 120V, 1-Phase & 3-Phase Main Panel? The following wiring diagram shows all the three phase loads and 3-Poles

3 Phase Distribution Board Layout and Wiring Diagram / Three phase

© 2026 BAGYOU FIBRE NETWORKS - All rights reserved

In this video, I try to explain three phase distribution board layout and wiring diagram. Three phase power supply is required, when the Power distribution requirement cannot be handled by a ...

3 phase distribution DB box wiring diagram

Three Phase Distribution DB box Connection.what is a three phase line?In electrical engineering three phase electric power systems have at least three conduc...

DIY Wiring a Three Phase Consumer Unit-Distribution Board and Wiring ...

Page Up The Practical Way of Wiring the Three Phase 60A Distribution Board with a MCCB. Wiring Diagram according to Old Colour Code The MCCB used here is a 3 Pole,60A unit. An MCCB with 4

Three (3) Phase Distribution Board Wiring Diagram and Connection

Hey, in this article we are going to see the Three (3) Phase Distribution Board Wiring Diagram and Connection Procedure. The three-phase distribution board is used to distribute power

Three Phase Distribution Board Wiring Diagram

The three phase distribution board wiring diagram shows how the current flows between the various components in the three phase distribution board. It also includes details of the ratings of

3 Phase Distribution Board Wiring Diagrams PDF

Three Phase (3 Phase) Distribution Board -Consumer Unit- Wiring Diagram PDF- DIY Wiring "Electric and magnetic forces. May they live for ever, and never be forgot, if only to remind us that the science

© 2026 BAGYOU FIBRE NETWORKS - All rights reserved

Contact Us

Continue your research online:

Website: https://bagyou.es
Technical inquiry: https://bagyou.es/project-enquiry.html

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.



© 2026 BAGYOU FIBRE NETWORKS - All rights reserved